

EXPERIMENT # 3

BJT CURRENT MIRRORS

THEORETICAL BACKGROUND

- Current Mirrors are used as current sources to bias circuits on ICs because they use fewer components and hence require little chip area.
- Two current mirror circuits will be studied in this lab:
 - Wilson Current Source
 - Widlar Current Source
- The use of current mirrors to provide bias current to the other circuits is shown in *figure # 1*. In this figure two stages of current mirrors are supplying bias current to two different circuits. The stages in a current mirror circuit can be extended if more circuits are needed to be attached for current biasing

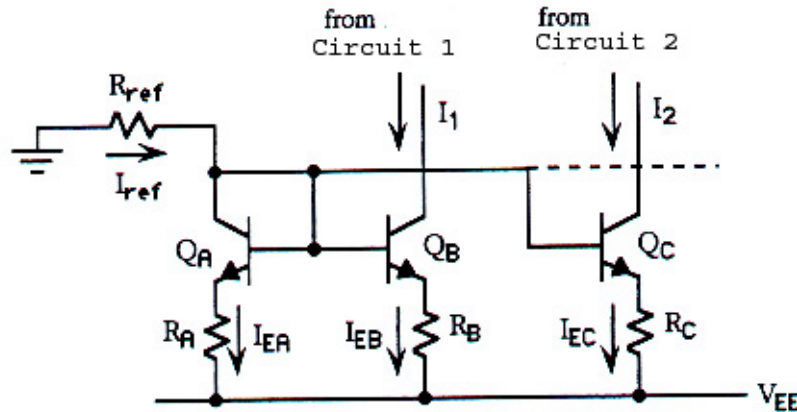


Figure # 1

- In a current mirror circuit, all transistors are matched; they have same value of current gain β_f and same size so for the equal value of V_{BE} , the collector currents I_C are equal.
- In *figure # 1*, if the small base currents are ignored and transistors are in active region then

$$I_{ref} = \frac{-(V_{EE} + 0.7)}{R_A + R_{ref}} \quad (1)$$

- Also applying *KVL* in the lower loop of transistors *A* and *B*, one can write

$$-I_{EA}R_A + I_{EB}R_B + V_{BE_B} - V_{BE_A} = 0 \quad (2)$$

- Again, ignoring small base currents of transistors A and B , $I_{EA} = I_{ref}$ and $I_{EB} = I_1$, (2) can be written as

$$-I_{ref}R_A + I_1R_B + V_{BE_B} - V_{BE_A} \approx 0 \quad (3)$$

- Using diode *voltage-current* relationship, the current through the forward biased *emitter-base* junction of the transistors can be written as

$$I_D = I_S [e^{\frac{V_D}{V_T}} - 1] \quad (4)$$

- Since in forward bias, I_S (saturation current) is small, hence above equation can be written as

$$I_D \approx I_S e^{\frac{V_D}{V_T}} \quad (5)$$

- Since transistors are matched, hence $I_{SA} = I_{SB}$, $V_D = V_{BE}$, $I_D = I_E$ and assuming $\eta=1$, using (3) and (5), I_1 can be written as

$$I_1 = I_{ref} \frac{R_A}{R_B} + \frac{V_T}{R_B} \ln \frac{I_{ref}}{I_1} \quad (6)$$

where $V_T = 26\text{mV}$ at room temperature

- Equation (6) is the relation for *Wilson Current Mirror*.
- If I_1 and I_{ref} are very close in value, $\ln \frac{I_{ref}}{I_1} \approx 0$ and

$$\frac{I_1}{I_{ref}} \approx \frac{R_A}{R_B} \quad (7)$$


- If very low biased current is required, *Widlar Current Mirror* can be used. It is obtained by removing R_A from *figure #1*. With R_A removed, (6) can be written as

$$I_1 = \frac{V_T}{R_B} \ln \frac{I_{ref}}{I_1} \quad (8)$$

which is the defining relationship of *Widlar Current Source*

PRELAB (1% of the Total Grade)

- Derive equation (6), using (3) and (5)
- Design Wilson Current source as shown in *circuit # 2* for $I_{ref}=1$ mA i.e. first calculate the values of $R_{ref}+R_A$ using (1), then choose some suitable value for either R_{ref} or R_A and calculate the other resistor (keep R_{ref} larger than R_A). Now choose two values of I_I less than $I_{ref}=1$ mA and two values of I_I greater than $I_{ref}=1$ mA and for each case find values of R_B by solving (6). Calculate the value of V_{CE} for transistor Q_B for each of the four values of I_I and make sure that your transistor is in active region, i.e., $V_{CEB} \gg 0.2V$. Use $V_{EE} = -10V$ and any value of R_B up to $10K\Omega$. Since R_1 does not appear in either (1) or (6) so you can choose a suitable value for it without effecting your results (for e.g. $R_1=3K\Omega$)
- Now design a Widlar Current Source by removing R_A from Wilson source and again calculate the value of R_{ref} for $I_{ref}=1$ mA. As it can be seen from (8) that for Widlar source I_I can not exceed I_{ref} , hence choose two values of I_I less than $I_{ref}=1$ mA and for each value, calculate the value of R_B from (8) as you did it for Wilson source. Calculate the value of V_{CE} for transistor Q_B for each of the four values of I_I and make sure that your transistor is in active region, i.e., $V_{CEB} \gg 0.2V$.

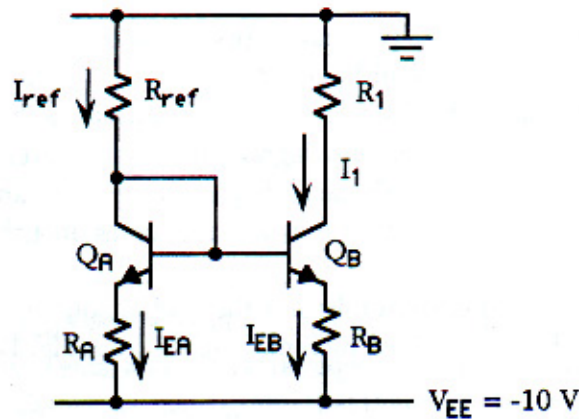

Circuit # 2

LAB PROCEDURE

- Implement *step # 2* of prelab. For each case measure:
 - I_I
 - I_{ref}
 - V_{CE} of transistor B to make sure that it is not in the saturation region.

2. Implement *step # 3* of the prelab and measure the same quantities as you did for Wilson source.

DATA ANALYSIS

- Compare and analyze the measured and calculated values of Wilson and Widlar current sources from equations (1), (6) and (8). Discuss and interpret your results in detail.

NOTE:

Label the transistors that you used in this lab to use in the next lab